▶ TASK Use wiring diagrams during the diagnosis (troubleshooting) of electrical/electronic circuit problems.

Additional Task

Time off_

Time on_

Total time_

CDX Tasksheet Number: N/A

NOTE This task requires diagnosis of an electrical problem. Please ask your instructor/supervisor to assign you a vehicle that qualifies for this task and several that follow.

- 1. List the customer concern/complaint:
- 2. Which electrical circuit(s) are involved?
- 3. How many circuit protection devices are there in this circuit? _____
 - a. List the circuit protection devices in this circuit:
 - b. List the circuit control devices in this circuit:
 - c. Which side of the load(s) is controlled?

4. Diagnose the fault and list each test and its result:

5. Determine any necessary actions:

6. Have your supervisor/instructor verify satisfactory completion of this procedure, any observations found, and any necessary action(s) recommended.

Performance Rating		CDX Tasksheet Number: N/A		
0	1	2	3	4
Supervisor/instructor signature				Date

NOTE Continue with the diagnosis of the electrical fault from the previous task.